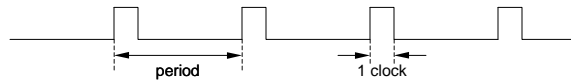


Timers


Uses

- timed interrupt


- pulse generator



- frequency generator

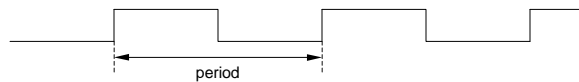

- pulse-width modulation (PWM)

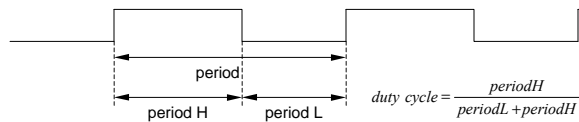

Timer Characteristics

Size (number of bits)

for flexibility want to be able to generate both high and low frequencies

Example: clock is 20 MHz
 8-bit counter minimum $f = 78 \text{ KHz}$
 16-bit counter minimum $f = 305 \text{ Hz}$
 24-bit counter minimum $f = 1.2 \text{ Hz}$

can use prescaler to reduce number of counter bits

Compare Registers

vary timing by comparing Count Register with a compare register
 same number of bits as Count Register
 generally Count Register counts up and resets to 0 when matches value in a compare register


Additional Features

one-shot or continuous mode
 generates interrupts

µC Timer Examples


Number of Timers	
PIC10F200	1
68HC05B4	2
PIC16C55	3
ATMega64	4
AT91RM9200	6
TMS470R1A768	32



ATMega Timer


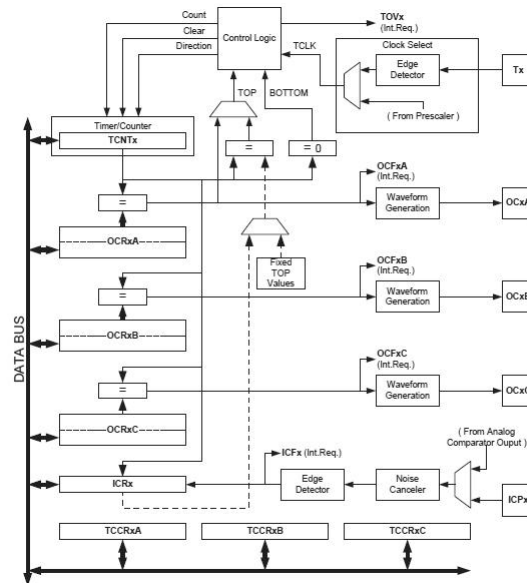


Timer Design

Basic Timer Counter

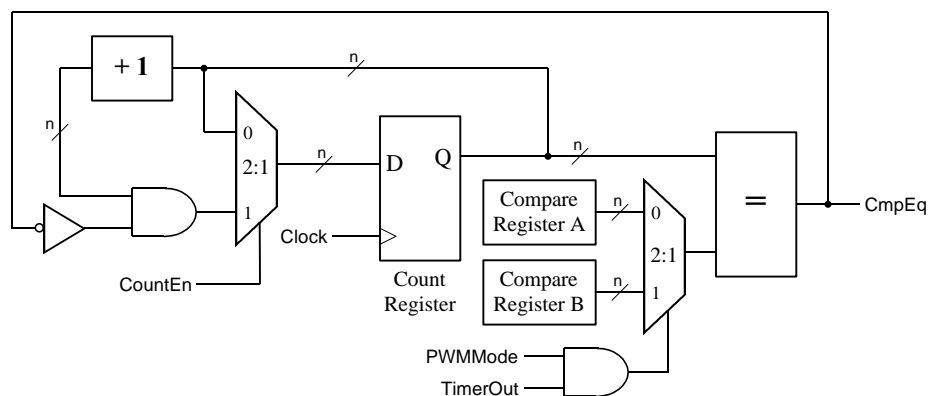


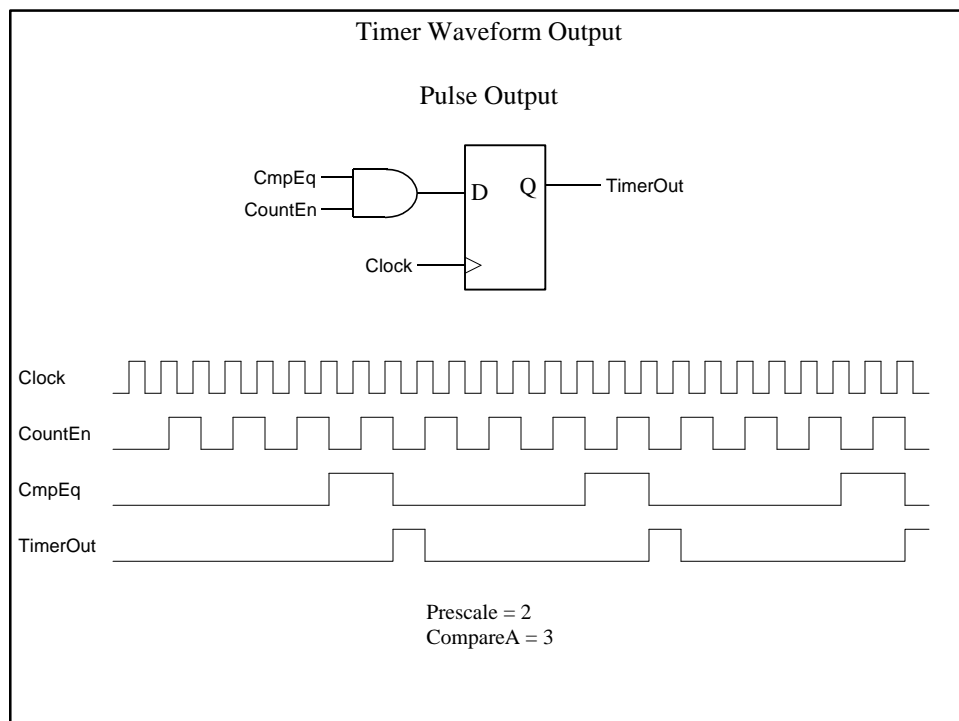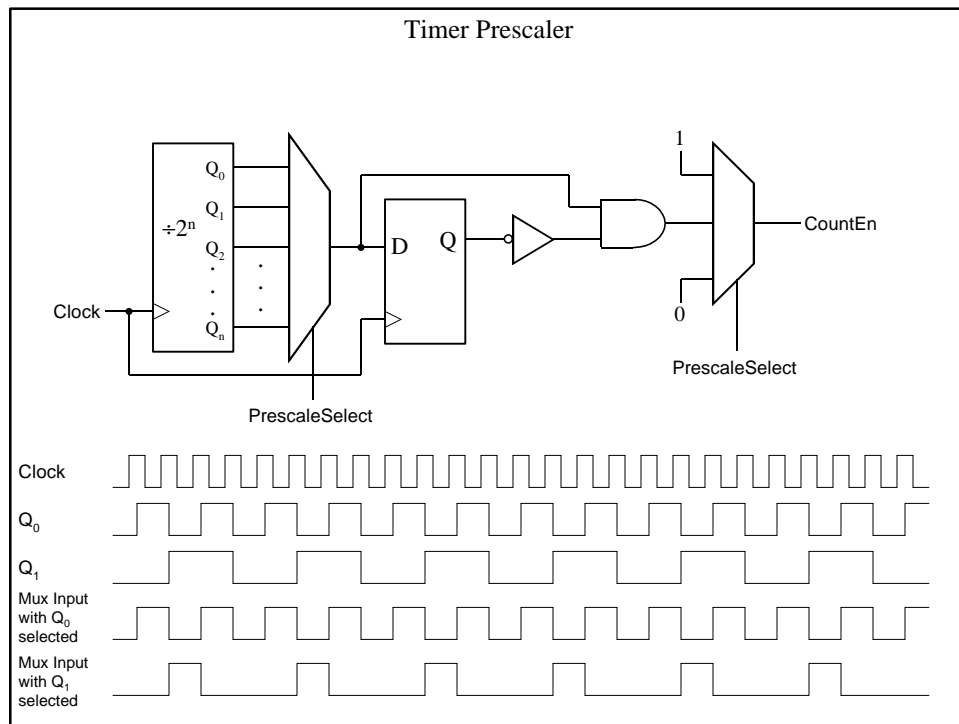

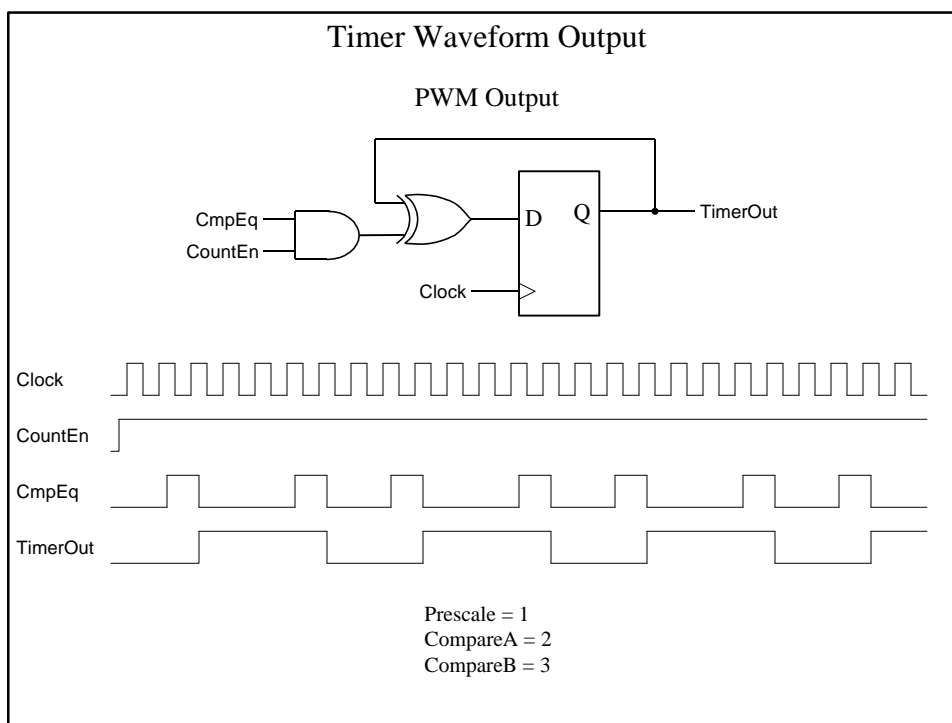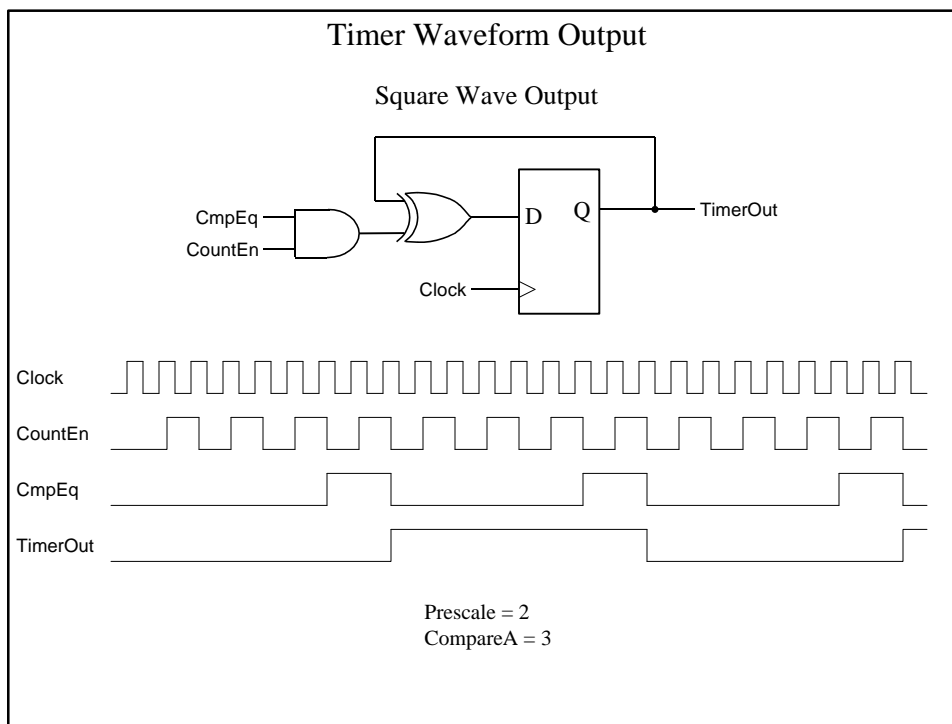


Timer Waveform Output

Pulse Output

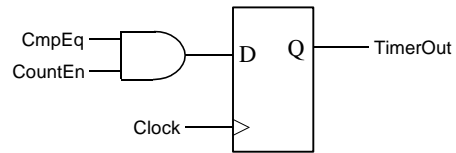

Square Wave / PWM Output

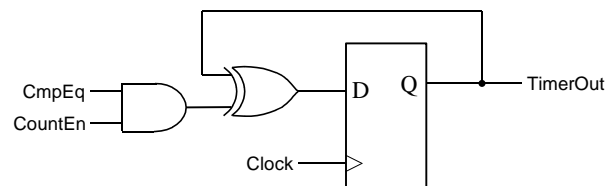

Timer Status & Interrupts

